



**BSc (Hons) in Computer Engineering  
Laboratory Practical  
ET1102- Basic Electronics**

**Experiment #3 Combinational and Sequential  
Logic Circuit**

Name:	.....	
Index No	.....	
Intake	.....	
Date	.....	
Instructor Name and Signature:	.....	
Comments	..... ..... .....	<b>Grade</b>

**Objectives:**

- After successfully completing this experiment you would be able to;
- (a) Get familiar with Logic Gates and Flip Flops in commercially available ICs.
  - (b) Identify the pin connections of ICs using data sheets.
  - (c) Build simple combinational and sequential circuits.
  - (d) Use logic probe to check the logic level in digital circuits.
  - (e) Use logic Pulser to apply clock pulses.

**Equipment required:**

**Components required:**

+5V Dc power supply  
Waveform Generator  
Logic Probe  
Protoboard  
Logic Pulser


IC 7400  
IC 7486  
IC 7473 (2 nos)  
LEDs (6 nos)  
1.2K resistor

---

**Procedure :**

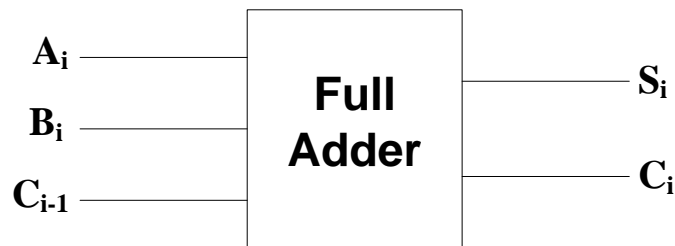**a) Full Adder**

Full Adder has 3 inputs and 2 outputs.  $A_i$  and  $B_i$  are the two binary bits to be added and  $C_{i-1}$  is the Carry coming from the  $i-1^{\text{th}}$  bit. Two outputs are Sum and Carry for the  $i^{\text{th}}$  bit.



➤ Draw the Truth Table for the full adder and obtain expressions for  $S_i$  and  $C_i$ .

$A_i$	$B_i$	$C_{i-1}$	$S_i$	$C_i$


$S_i =$

$C_i =$

- Build a full adder using XOR gates and NAND gates. You may use the data sheets provided to find the pin connections of the ICs.
- Verify the Truth Table for the full adder by giving inputs and measuring the output with the logic probe.

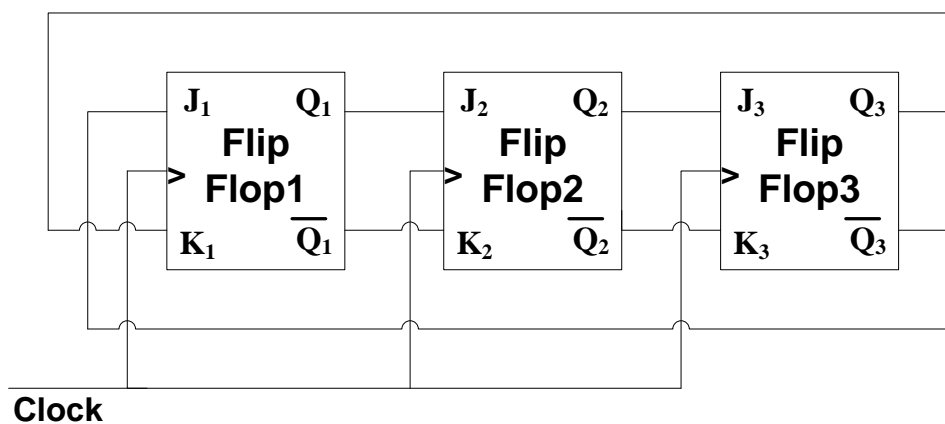**b) Sequential Circuits with a moving band of lights.**

- Connect the following circuit using JK Flip Flops. You may use the data sheets provided to find the pin connections of the ICs.



- Connect the 6 LEDs to  $Q_1$ ,  $Q_2$ ,  $Q_3$ ,  $\overline{Q_1}$ ,  $\overline{Q_2}$ ,  $\overline{Q_3}$  pins respectively. The negative pins of LEDs should be connected together and then connected to ground through the 1.2K resistor.
- Connect the clear pins of the flip-flops to ground momentarily and then keep it permanently connected to +5 V.
- Apply clock pulses to the clock input of flip-flops using the Logic Pulsar (set the pulsar frequency to 0.5 Hz) and find the sequence of the ON LEDs.

Clock Pulse	LEDs					
	1	2	3	4	5	6


- Apply a pulse train of + 5V amplitude and 10 Hz frequency to the clock input of flip flops and observe the effect of moving band of lights.

## Performance Evaluation

### Experiment: Combinational and Sequential Logic Circuit

	Evaluation Aspect	Marks
1	Preparation	
2	Neatness of Work	
3	Familiarity with Lab Equipment	
4	Completion of Work	
5	Capability	
6	Accuracy of Readings/ Observations	
7	Answers given to Questions	
8	Discipline	
	Total	

Marks are awarded on a 0-10 scale for each aspect

Excellent	Very Good	Good	Fair	Poor	Very Poor
10	9 – 8	7 – 6	5 – 4	3 – 2	1 – 0

Name of the Instructor: .....

Signature: .....

Date: .....