



**BSc (Hons) in Computer Engineering
 Laboratory Practical
 EE1012- Electrical Engineering**

**Experiment #5 Serial Parallel Networks and
 Kirchoff's Laws**

Name:		
Index No		
Intake		
Date		
Instructor Name and Signature:		
Comments	<table border="1"> <tr> <td>Grade</td> </tr> </table>	Grade
Grade			

Objectives

- To identify series, parallel and series-parallel networks.
- To become familiar with the application of Kirchoff's Laws

Experiment background

From the experiments given so far, it should be easy for you to identify both series and parallel circuits. But there is another type of circuit that has branches, like parallel circuits, and series loads or elements, like series circuits. This is called a series-parallel network since it is a combination of the others.

There are many circuits that are so complex that they cannot be solved by just using the Ohm's Law. These circuits have many branches or many power sources, and Ohm's Law would be either impractical or impossible to use on them. Methods for solving complex circuits have been developed, and are based on the experiments of a German physicist, Gustav Kirchhoff. In 1857, Kirchhoff developed two conclusions, known as Kirchhoff's Laws, can be stated as follows:

- Kirchhoff's voltage law
- Kirchhoff's current law

Pre-lab study

- Serial-parallel networks
- Kirchhoff's laws

Equipment used

- KL-21001 module
- Breadboard module
- Jumper wires, crocodile clips and jacks
- 2x Resistors of 1 kW
- 1x Variable resistor of 5 kW

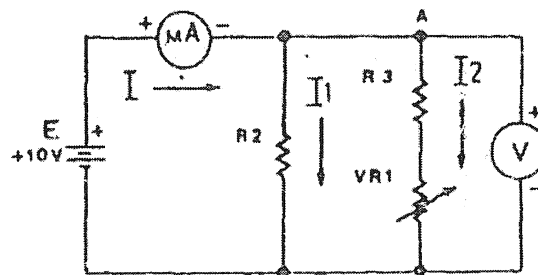


Figure 2 - Circuit to test Kirchhoff's current law

7. Adjust VR1 to 1 kW and calculate the total resistance R.
8. Measure and record the voltage of voltmeter.
9. Adjust VR1 to maximum and observe the reading of voltage on the voltmeter.
10. Adjust VR1 to 0 W. Measure and record the total current

Procedure

1. Set the on the main unit KL-21001, and place the breadboard on it.
2. Complete the experiment circuit using jumper wires, resistors and the breadboard according to Figure 1 to test Kirchoffs voltage law. Use a 1 kW resistor as R1.

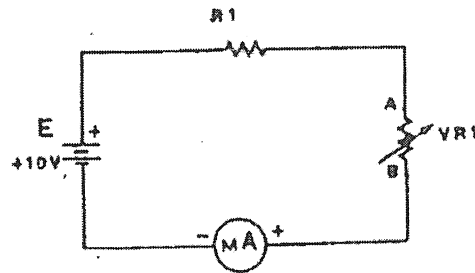


Figure 1 - Circuit to test Kirchoff's voltage law

3. Adjust VR1 to 1 kW and apply +10V as voltage source. Calculate total resistance and current.
4. Insert the milliammeter in the circuit as shown in Figure 1, measure and record the current I.
5. Adjust VR1 to 500 W and repeat steps 3 and 4. Record the results in observation and readings section.
6. Construct the circuit as shown in Figure 2 to test the Kirchoff's current law. Use 1 kW resistors for R2 and R3.

Experiment	Serial Parallel Networks and Kirchhoff's Laws	Official Seal
Name of Student		
Registration Number		
Intake		
Date of Performance		

For official use only. Do NOT fill.

Marks	
--------------	--

Experiment Report

Introduction

Kirchhoff's Voltage law

Kirchhoff's Current Law

Calculations

Step 3

Calculate the total resistance $R = R1 + VR1 =$ _____ W

Calculate the current $i =$ _____ mA

Step 5

Total resistance $R = R1 + VR1 =$ _____ W

Calculate the Current $I =$ _____ mA

Step 7

$$R = \text{_____} \text{ W}$$

Step 10

Calculate the branch currents

$$I_1 = \text{_____} \text{ mA}$$

$$I_2 = \text{_____} \text{ mA}$$

Calculate the total current by using Kirchhoff's current law.

$$I = I_1 + I_2 = \text{_____} \text{ mA}$$

Observations and readings

Step 4

$$I = \text{_____} \text{ mA}$$

Step 5

$$I = \text{_____} \text{ mA}$$

Step 8

$$E = \text{_____} \text{ V}$$

Step 9

$$\text{Variation in } E = \text{_____} \text{ V}$$

Step 10

$$I = \text{_____} \text{ mA}$$

Discussion

Step 3

What is the type of the circuit of Figure 1 (series or parallel)

Step 4

Is there agreement between the measured current in step 4 and calculated current in step 3? If not why?

Step 6

What is the type of the circuit of Figure 2 (series or parallel)

Step 8

Is the measured voltage value equal to the voltage value supplied in step 3? Why?

Step 9

Does the voltage measured change when VR1 changes? Why?

Step 10

Is there agreement between your measured and calculated current values? Why?

What is the importance of Kirchhoff's laws?
